


ECN-252 Lab 7

For questions: contact Dr Sparsh (sparshfec@iitr.ac.in)

Hint: Use 2's complement number representation for all the numbers. You can use the adder/multiplier/comparator from the previous assignments and use them as building blocks. You don't have to test them again or show their outputs.

Part 1 (ReLU function)

 - i) We need to detect whether a number is positive or not. You can use a comparator for this (hint: in fact it is much simpler than that!). The input number is 4-bit. **NOTE: you don't need to submit a circuit for this. Just write the Boolean logic or reasoning for achieving this functionality (max 2 sentence).**
- ii) The following function is called ReLU and it is shown in the figure below.
 $y = \max(0, x)$.
Although simplistic, it is used heavily in neural network. Implement a circuit to achieve this function. The input x is a 4-bit number,



Part 2 (Training an overly simplistic perceptron):

Consider the training algorithm of a perceptron

```
for each  $0 \leq i \leq n$  in parallel
  if  $t = x_i$  then
     $w_i := w_i + 1$ 
  else
     $w_i := w_i - 1$ 
  end if
end for
```

Here, for sake of simplicity, we will assume that $n=1$ and instead of 0, the value of i begins with 0. In other words, there is only one perceptron. Thus, there is only one value of x , one value of w and one value of t .

Design a circuit to implement the training algorithm. The weight (w) is 4-bit and is fixed to be 0010. The input (x) needs only 2-bit because its value can be either +1 or -1. The output (t) is also 2-bit and its value can be either +1 or -1. As you can see, for 2 possible values of x and 2 possible values of t , we have a total of 4 combinations to evaluate (weight is already fixed). Thus, we do NOT have 16 possible combinations, but just 4 combinations.

Hint: A very important point to note here is that although x is using 2-bit for its storage, it can have only 2 distinct values. Thus, the remaining 2 combinations are not used. The same is also true for t .

Hint: In the comparator, we only need to check whether t is equal to x or not. Hence, for both $t > x$ or $t < x$, the action taken is same.

Part 3 (Doing inference with an overly simplistic perceptron):

Design a small circuit to implement a simple pattern recognition where given two co-ordinates (x , y) as inputs to the circuit, the circuit will tell if the given point is above or below a straight line. Straight line equation to be used is given in the table. Show your results for two test points – above and below the line. Choose points such that you don't exceed the 3 bit (for the multiplier) or 7 bit (for the sum) integer limit. (If you can't remember how to check this, see note below the table)

(This exercise is actually showing an over-simplified example of a neural network or a perceptron. Of course, we don't really need a neural network for this, however this shows how more complex networks may be realized using simple multiplication and addition as their building blocks. Adapted from the tutorial- <https://natureofcode.com/book/chapter-10-neural-networks/>)

There are 8 sets of problem (4 for ECE, 4 for CSE). To select within set 1 - 4, use mod (Roll No.,4)+1 and select the corresponding problem from the table below.

[For example, if your roll no. is 191112002, you should select $\text{mod}(191112002,4)+1 = 3$; i.e. set 3.]

Group	Straight line to be used for Part 3
ECE, Set 1	$2x-3y-6=0$
ECE, Set 2	$4x+3y=0$
ECE, Set 3	$x-2y=0$
ECE, Set 4	$2x+y+2=0$
CSE, Set 1	$x+3y-3=0$
CSE, Set 2	$2x-4y-4=0$
CSE, Set 3	$x-y=0$
CSE, Set 4	$x+y-1=0$

How to check if a point is above or below a given line?

Given any arbitrary line $ax+by+c=0$, a point (x_1 , y_1) is above the line if,

(a) $b > 0$ and $ax_1+by_1+c > 0$ OR (b) $b < 0$ and $ax_1+by_1+c < 0$