

Lab – 5


ECN – 252

19114001 | Abhinav Saini


Part 1 :

Half – Adder

Schematic

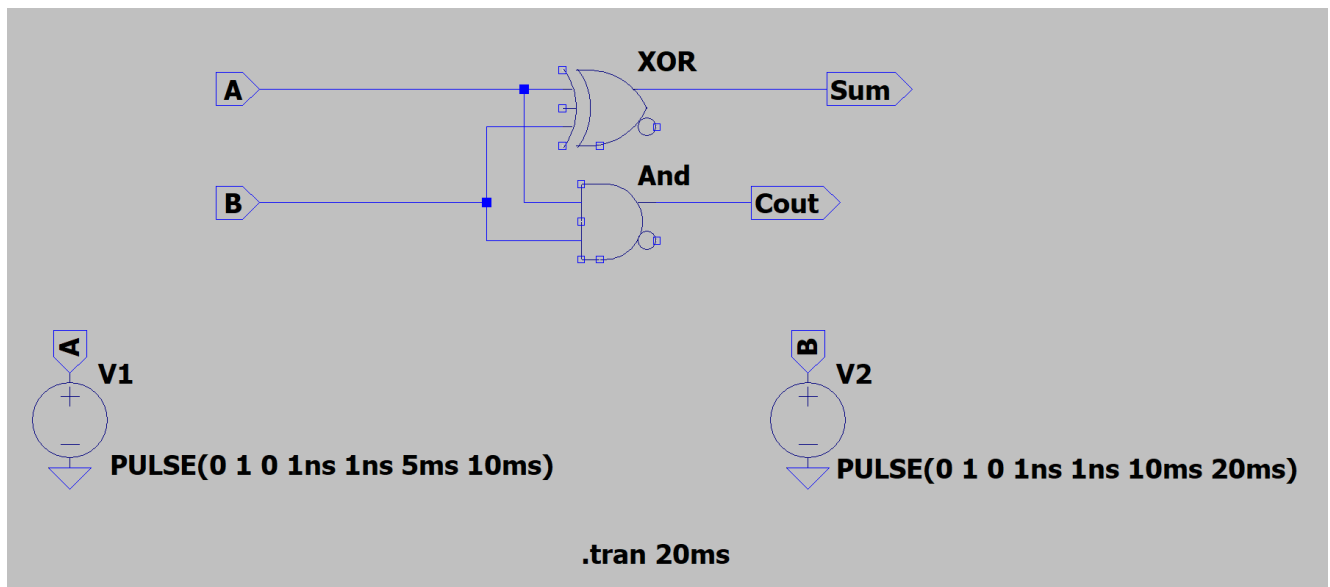


Simulation

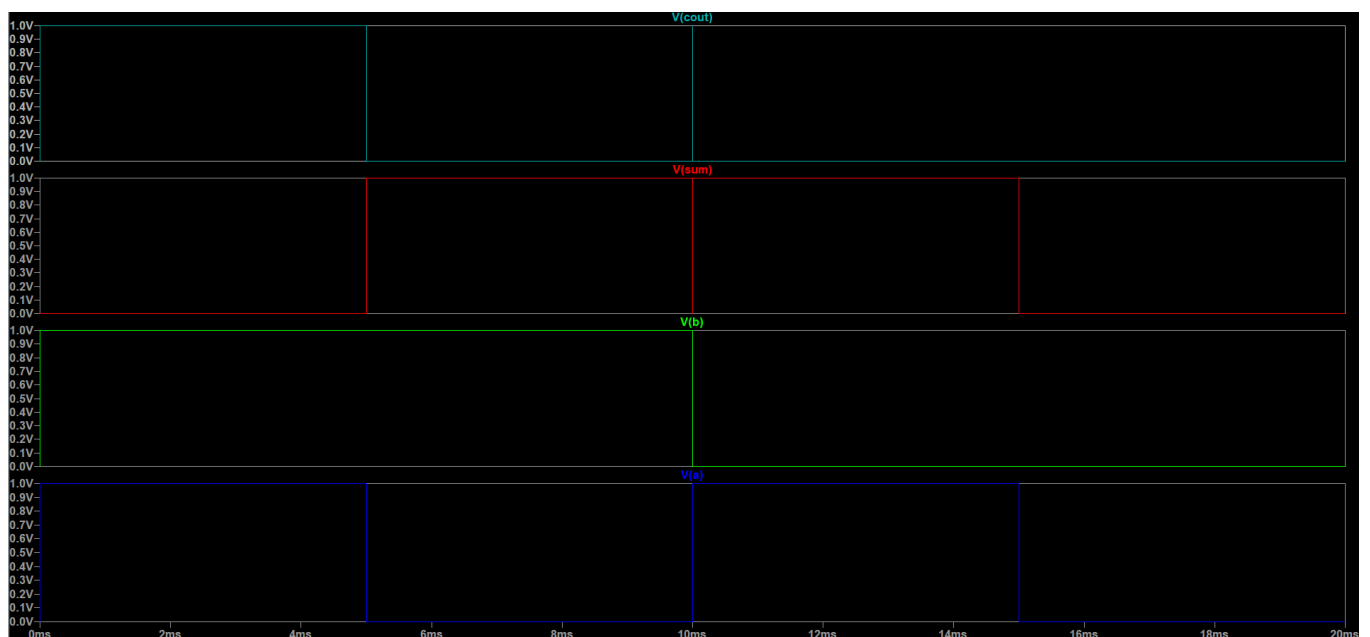


Full – Adder

Schematic

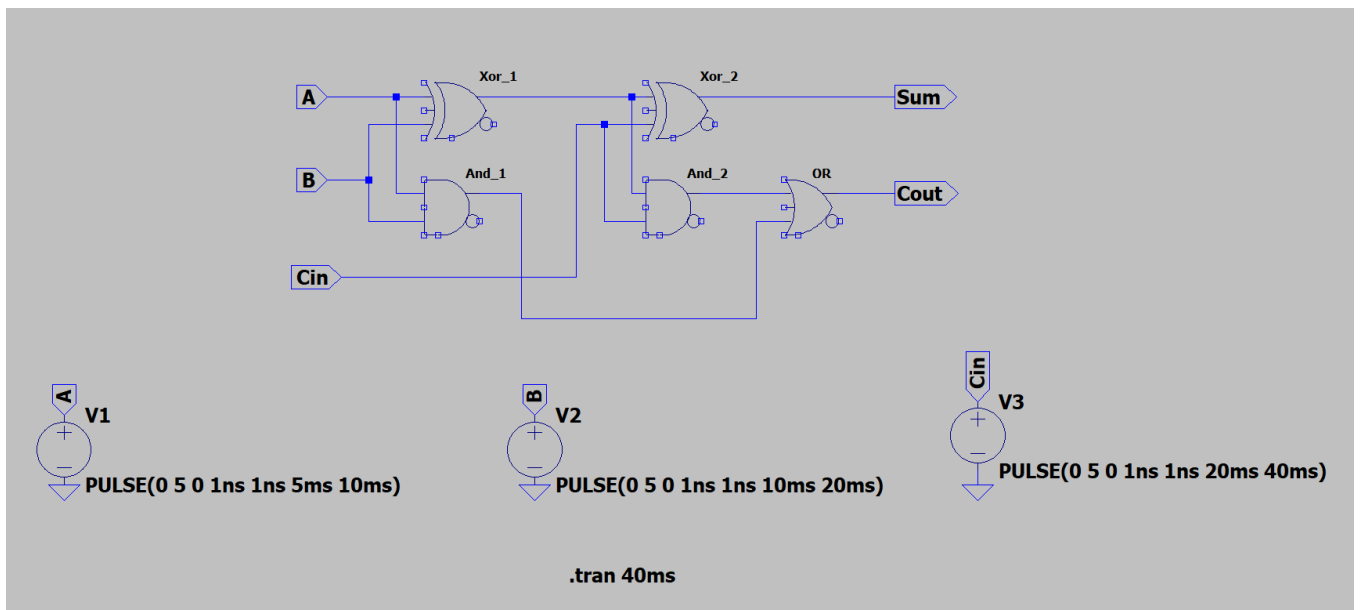


Simulation

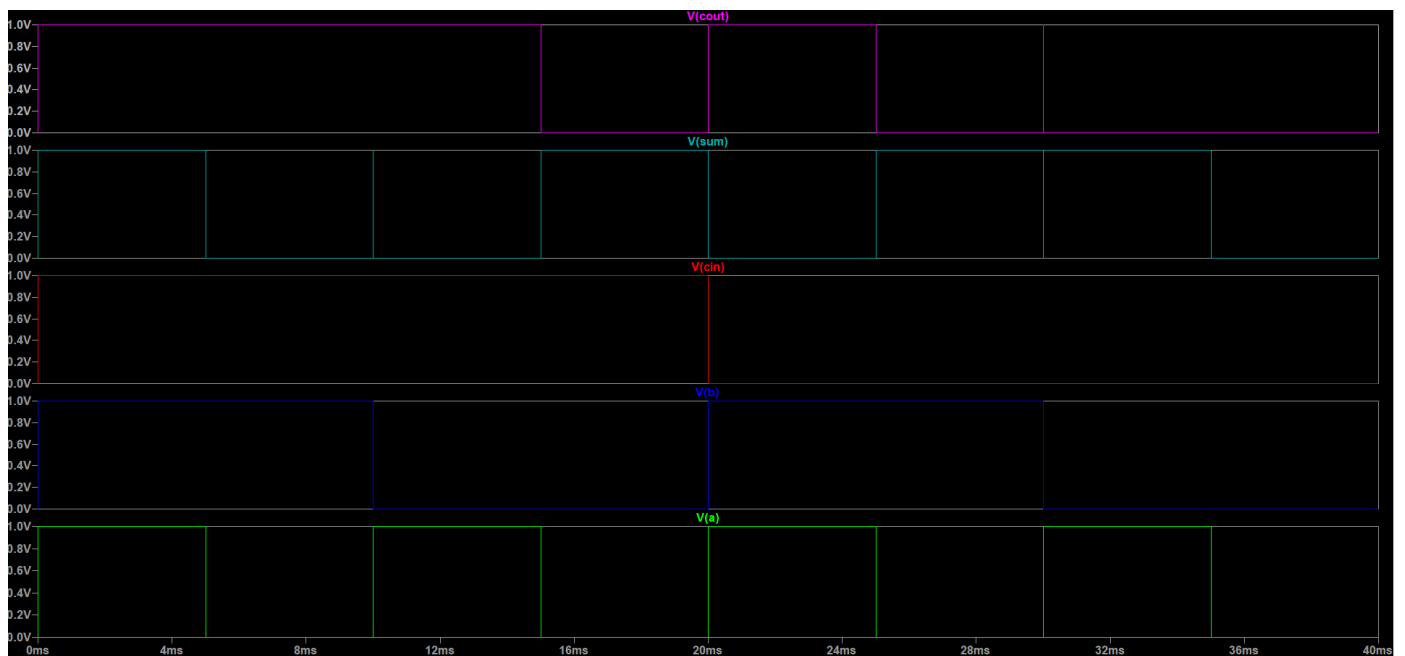

Part – 2 : 4-bit Multiplier


a) 1111 x 1111

Schematic

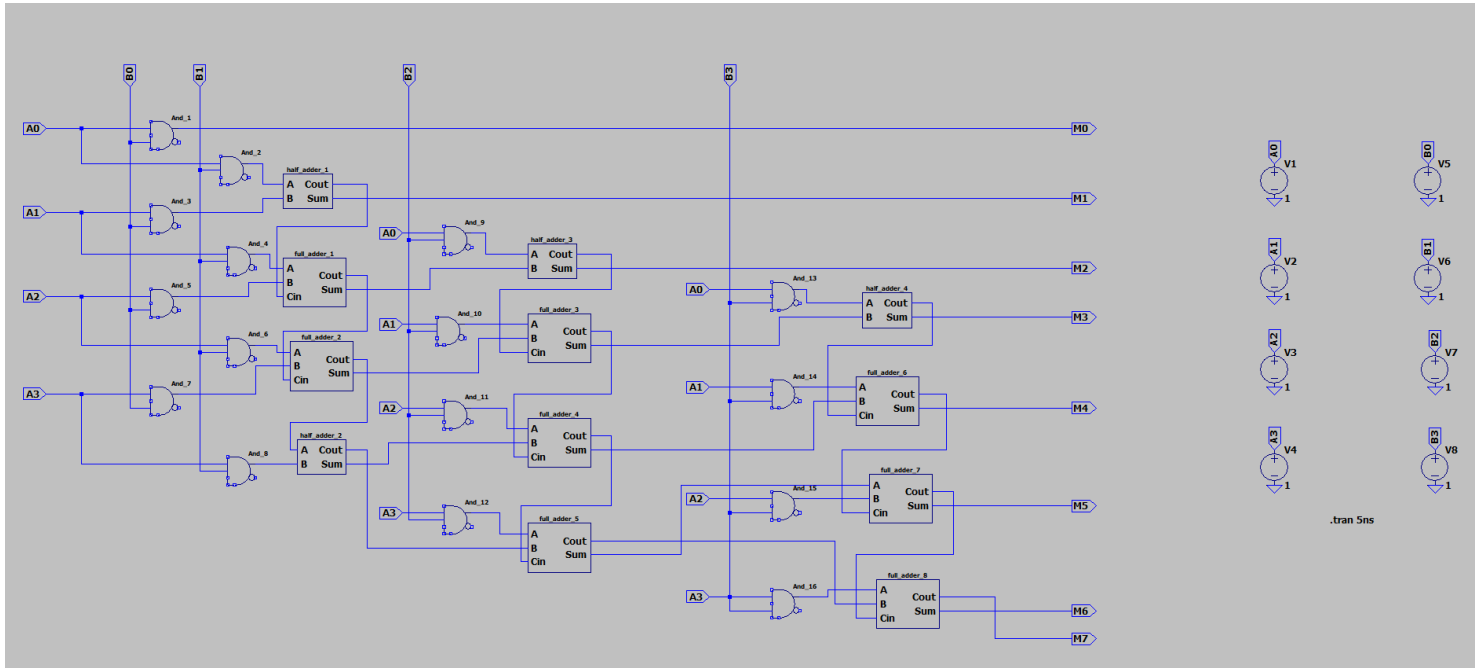


Simulation

Output - 11100001

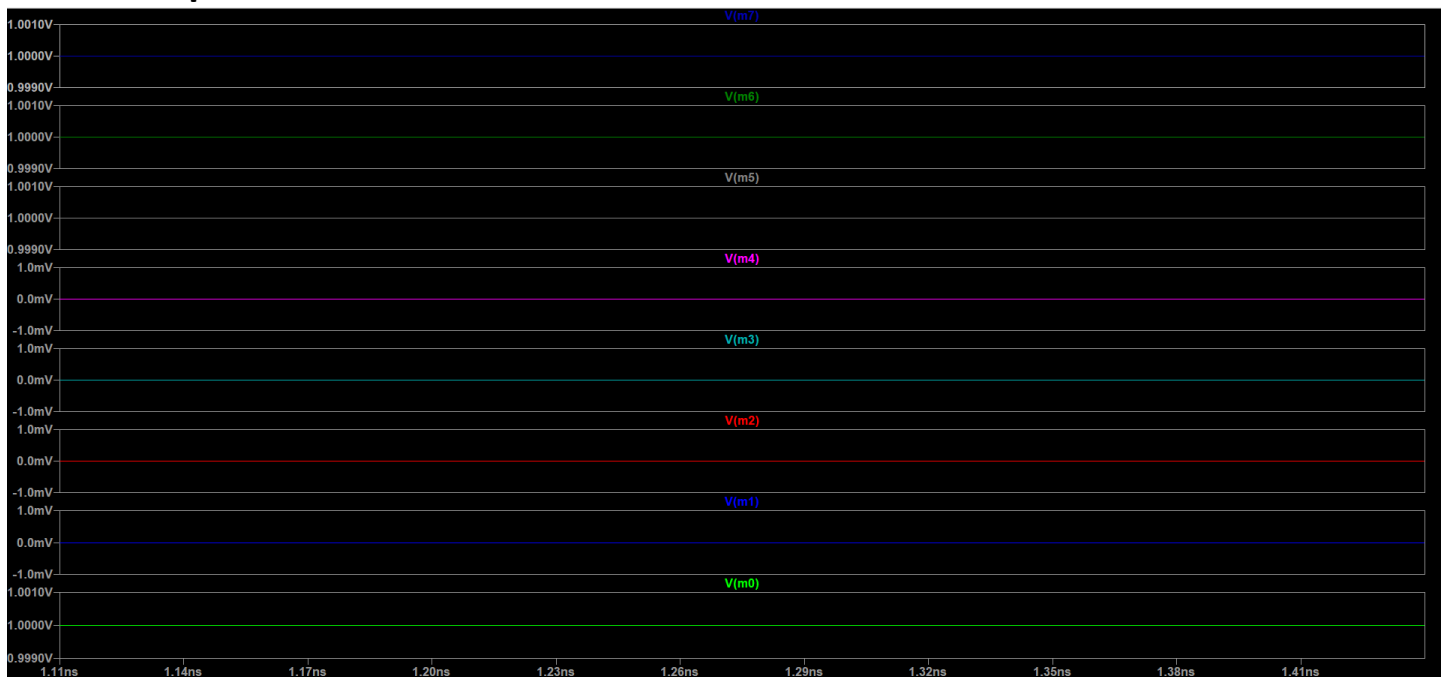

b) 1011 x 1110

Schematic

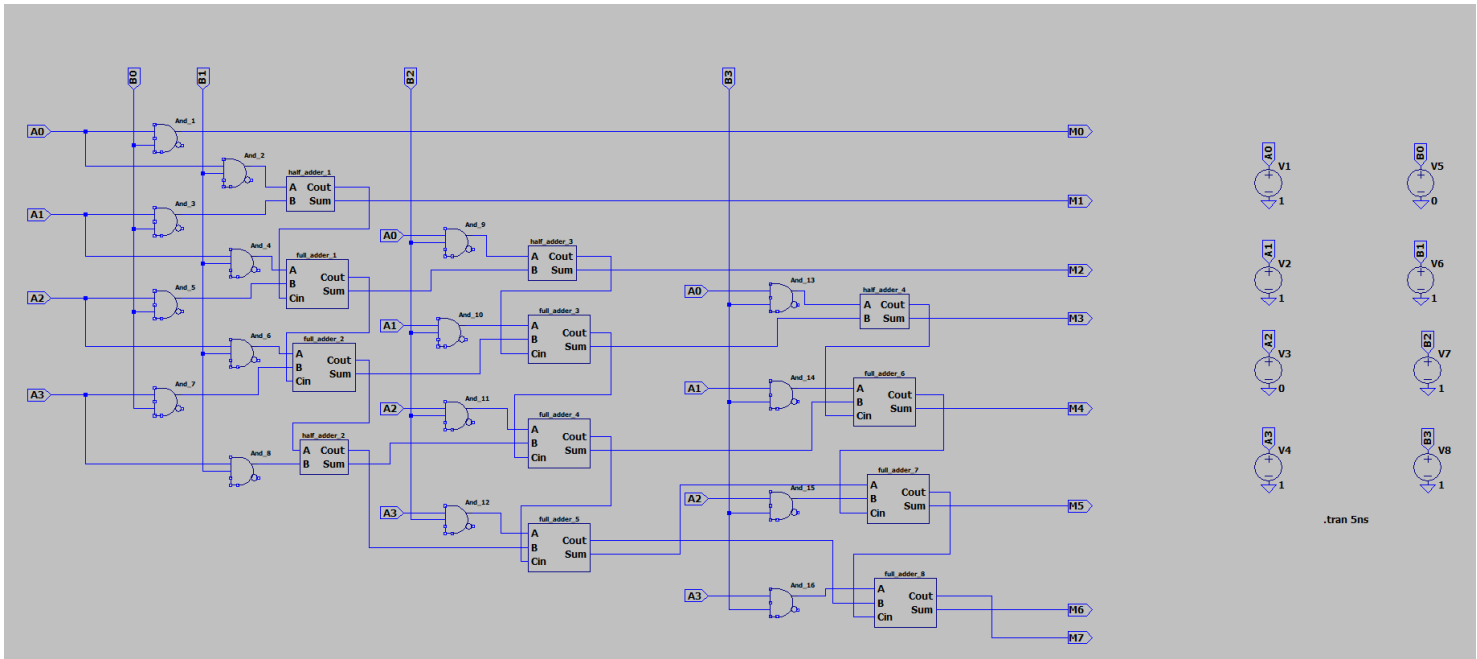

Simulation

Output - 10011010

