

Lab – 9

ECN – 252

19114001 | Abhinav Saini

Part 1: 4-Bit adder

Design

```
library IEEE;
use IEEE.std_logic_1164.all;
entity NAND_Gate is
Port (a,b: in std_logic; y: out std_logic);
end entity;
architecture NAND_Gate_Structure of NAND_Gate is
begin
    y <= not (a and b);
end architecture;
library IEEE;
use IEEE.std_logic_1164.all;
entity Full_Addder is
Port ( a, b, cin: in std_logic; sum, cout : out std_logic );
end Full_Addder;
architecture Full_Addder_Structure of Full_Addder is
component NAND_Gate Port (a,b: in std_logic; y: out std_logic);
end component;
signal S1, S2, S3, S4, S5, S6, S7: std_logic;
begin
    NG_1 : NAND_Gate Port map(a,b,S1);
    NG_2 : NAND_Gate Port map(a,S1,S2);
    NG_3 : NAND_Gate Port map(b,S1,S3);
    NG_4 : NAND_Gate Port map(S2,S3,S4);
    NG_5 : NAND_Gate Port map(S4,cin,S5);
    NG_6 : NAND_Gate Port map(S4,S5,S6);
    NG_7 : NAND_Gate Port map(S5,cin,S7);
    NG_8 : NAND_Gate Port map(S6,S7,sum);
    NG_9 : NAND_Gate Port map(S1,S5,cout);
end architecture;
library IEEE;
use IEEE.std_logic_1164.all;
entity Four_Bit_Addder is
    port( a, b      : in  STD_LOGIC_VECTOR(3 downto 0);
          ans       : out STD_LOGIC_VECTOR(3 downto 0);
          cout      : out STD_LOGIC              );
end Four_Bit_Addder;
architecture Four_Bit_Addder_structural of Four_Bit_Addder is
component Full_Addder port( a, b, cin: in  STD_LOGIC;  sum, cout:
out STD_LOGIC ); end component;
signal c0, c1, c2, c3 : STD_LOGIC;
```

```

begin
    c0 <= '0';
    b_adder0: Full_Adder port map (a(0), b(0), c0, ans(0), c1);
    b_adder1: Full_Adder port map (a(1), b(1), c1, ans(1), c2);
    b_adder2: Full_Adder port map (a(2), b(2), c2, ans(2), c3);
    b_adder3: Full_Adder port map (a(3), b(3), c3, ans(3), cout);
end architecture;

```

Testbench

```

LIBRARY IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity Four_Bit_Adder_tb is
end Four_Bit_Adder_tb;
architecture TEST of Four_Bit_Adder_tb is
    component Four_Bit_Adder    port( a, b : in  STD_LOGIC_VECTOR(3
    downto 0);


                                ans   : out
                                STD_LOGIC_VECTOR(3 downto 0);

                                cout  : out   STD_LOGIC



                                );
end component;
    signal a, b                : STD_LOGIC_VECTOR(3 downto 0);
    signal ans                  : STD_LOGIC_VECTOR(3 downto 0);
    signal cout                 : STD_LOGIC;
    begin
        U1: Four_Bit_Adder port map (a,b,ans,cout);
        process
        begin
            a <= "0000";
            b <= "0000";
            wait for 10 ns;
            a <= "1111";
            b <= "1111";
            wait for 10 ns;
            a <= "1010";
            b <= "0101";
            wait for 10 ns;
        end process;
    END TEST;

```

Waveform

 

Initially.

 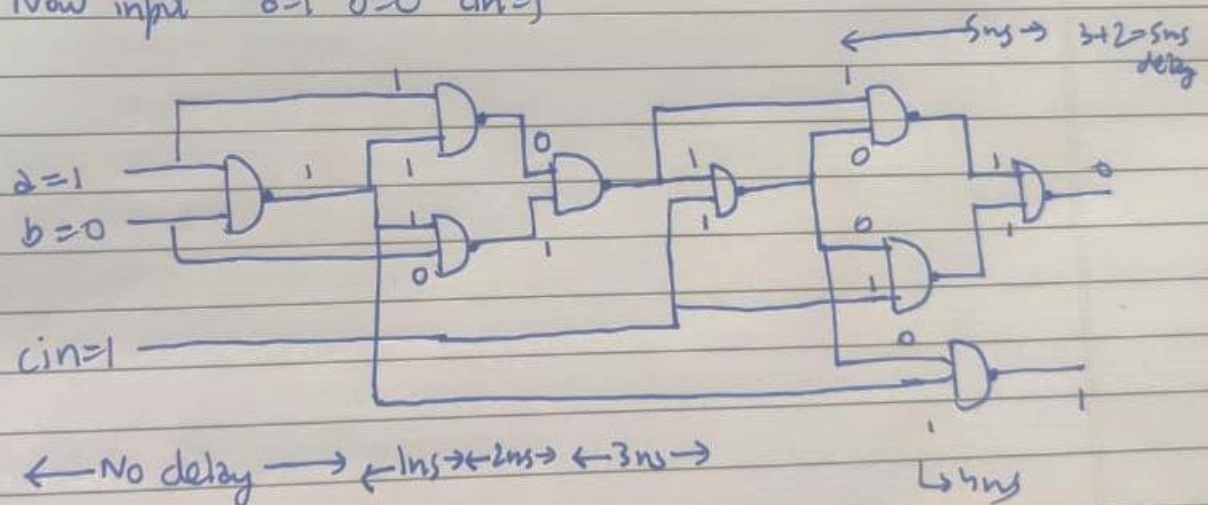Now input $a=1$ $b=0$ $cin=1$ 

Hence, theoretically, we get 5ns delay for sum bit i.e. the sum bit and 4ns delay for carry bit. Also is the same we obtain by simulations.

1-bit Adder with 1ns delay in Nand Gates

Design

```
library IEEE;
use IEEE.std_logic_1164.all;
entity NAND_Gate is
Port (a,b: in std_logic; y: out std_logic);
end entity;
architecture NAND_Gate_Structure of NAND_Gate is
begin
    y <= not (a and b) after 1 ns;
end architecture;
library IEEE;
use IEEE.std_logic_1164.all;
entity Full_Adder is
Port ( a, b, cin: in std_logic; sum, cout : out std_logic);
end Full_Adder;
architecture Full_Adder_Structure of Full_Adder is
component NAND_Gate Port (a,b: in std_logic; y: out std_logic); end
component;
signal S1, S2, S3, S4, S5, S6, S7: std_logic;
begin
    NG_1 : NAND_Gate Port map(a,b,S1);
    NG_2 : NAND_Gate Port map(a,S1,S2);
    NG_3 : NAND_Gate Port map(b,S1,S3);
    NG_4 : NAND_Gate Port map(S2,S3,S4);
    NG_5 : NAND_Gate Port map(S4,cin,S5);
    NG_6 : NAND_Gate Port map(S4,S5,S6);
    NG_7 : NAND_Gate Port map(S5,cin,S7);
    NG_8 : NAND_Gate Port map(S6,S7,sum);
    NG_9 : NAND_Gate Port map(S1,S5,cout);
end architecture;
```

Testbench

```
LIBRARY IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity Full_Adder_tb is
end Full_Adder_tb;
architecture Testbench of Full_Adder_tb is
component Full_Adder Port ( a, b, cin: in std_logic; sum, cout :
out std_logic);
end component;
    signal a, b, cin, ans, cout      : STD_LOGIC;
begin
    U1: Full_Adder port map (a,b, cin, ans,cout);

    process
```


```

begin

    a <= '0';
    b <= '0';
    cin <= '0';
    wait for 10 ns;
    a <= '1';
    b <= '0';
    cin <= '1';
    wait for 10 ns;
end process;
END Testbench;

```

Waveform

 

Part 2 : 2-bit Down Counter Design

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity Two_Bit_Down_Counter is
    Port ( clk: in std_logic;
          E: in std_logic;
          counter: out std_logic_vector(1 downto 0)
    );
end Two_Bit_Down_Counter;
architecture Down_Behavioral of Two_Bit_Down_Counter is
    signal counter_down: std_logic_vector(1 downto 0) := "11";
begin
    process(clk)
    begin
        if(rising_edge(clk)) then
            if(E='1') then
                counter_down <= counter_down - "01";
            end if;
        end if;
    end process;
    counter <= counter_down;
end Down_Behavioral;

```

Testbench

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity down_tb_counters is
end down_tb_counters;
architecture Down_Behavioral_tb of down_tb_counters is
    component Two_Bit_Down_Counter
        Port ( clk: in std_logic; E: in std_logic; counter: out
std_logic_vector(1 downto 0));
    end component;
    signal E,clk: std_logic;
    signal counter:std_logic_vector(1 downto 0);
begin
    dut: Two_Bit_Down_Counter port map (clk => clk, E=>E, counter
=> counter);
    process
    begin
        for i in 0 to 30 loop
            clk <= '0';
            wait for 1 ns;
            clk <= '1';
            wait for 1 ns;
        end loop;
    end process;

    process
    begin
        E <= '0';
        wait for 5 ns;
        E <= '1';
        wait;
    end process;
end Down_Behavioral_tb;
```

Waveform

