


Lab 2

ECN - 252


19114001 Abhinav Saini

Part – 1 Full Adder

Schematic

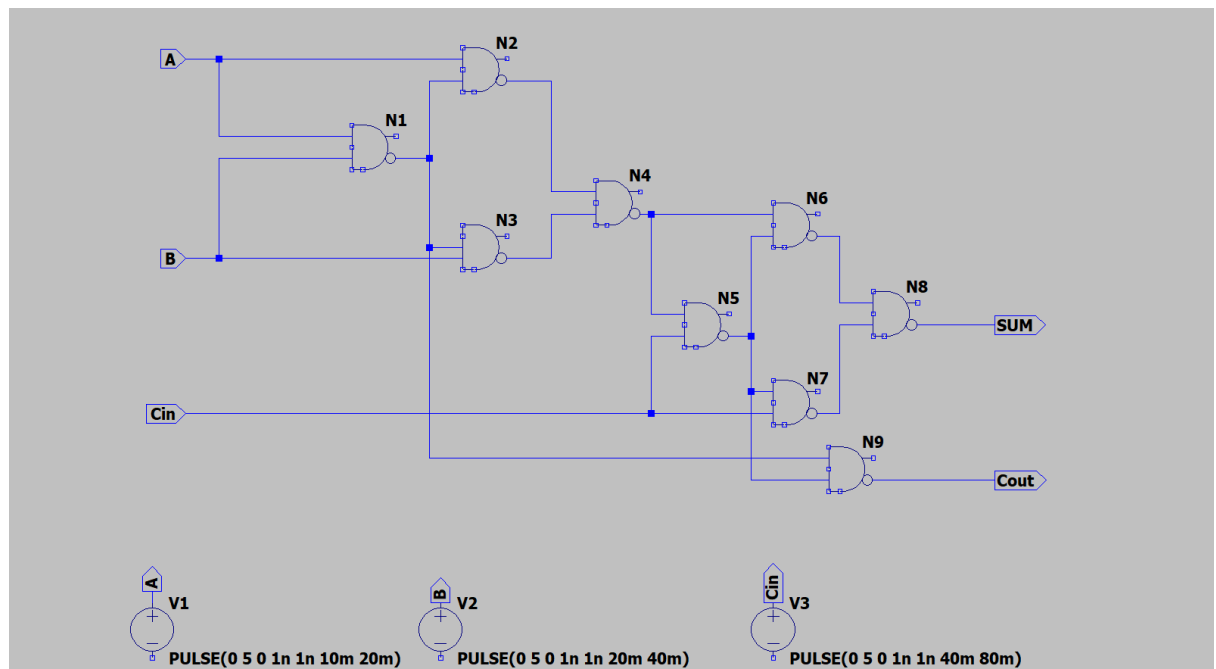


Simulation

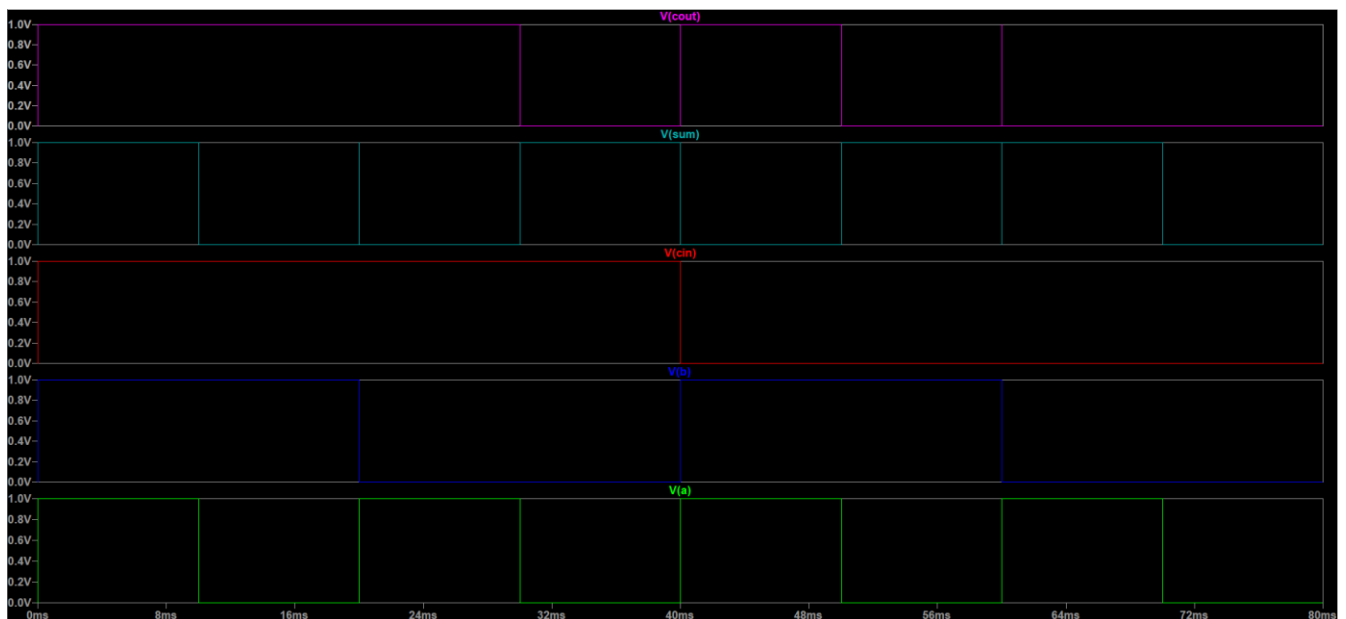


Part – 2 4-bit adder

Schematic

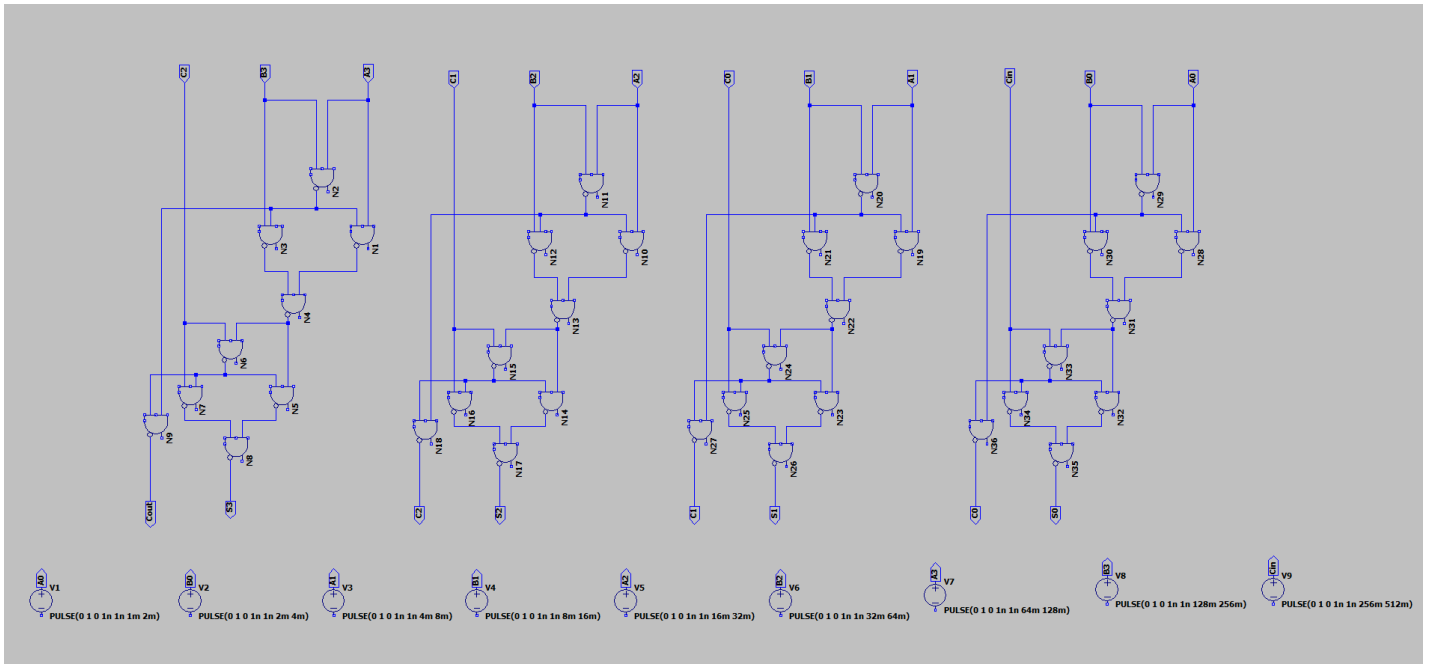

Part – 3 A = 1011 B = 0111, S = 0100

Schematic

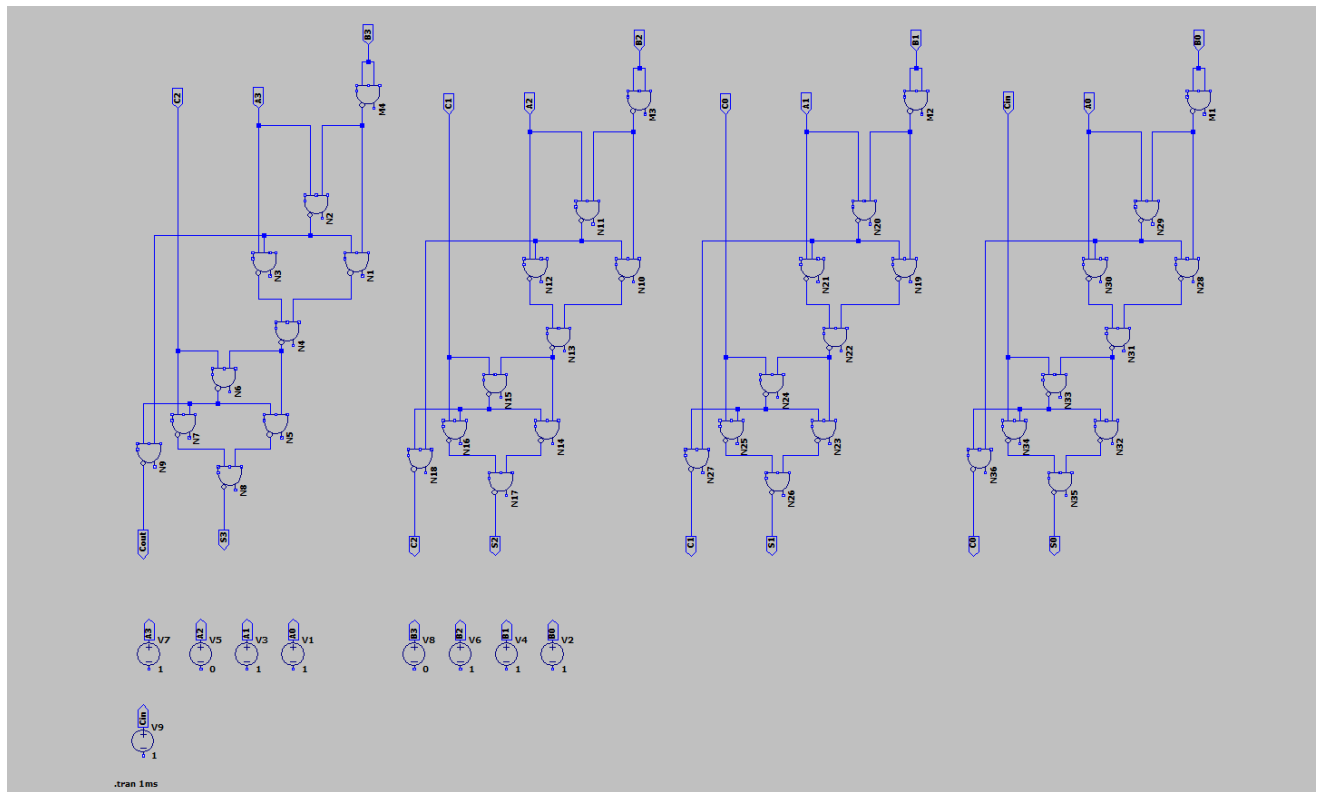

Simulation

