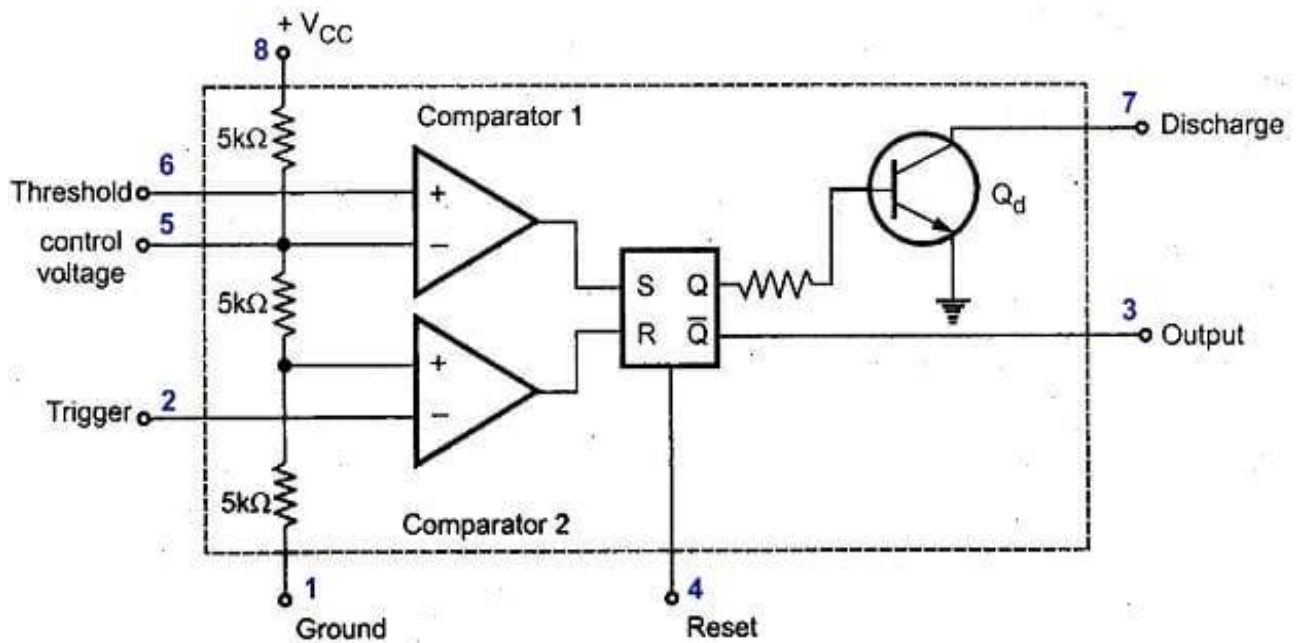


Lab 3

ECN – 252

19114001 | Abhinav Saini

Part 1 : Circuit Diagram of IC NE555 Timer



Part 2 :

Enrollment – 19114001

19114001 % 4 = 1. Therefore, **SET 2** of CSE Batch

Running Multi-Vibrator for frequency 2kHz and Duty cycle 50%.

$$\text{Duty Cycle} = t_H / t_H + t_L$$

$$\text{Thus, Duty Cycle} = 0.5 = R_A / (R_A + R_B)$$

$$\text{Hence } R_A = R_B$$

$$\text{Period} = 1 / \text{Freq.} = 0.693 * (R_A + R_B) * C \quad \text{where } C = 0.15\mu$$

$$\text{We get } R_A = R_B = 2.4\text{k-ohm}$$

Schematic

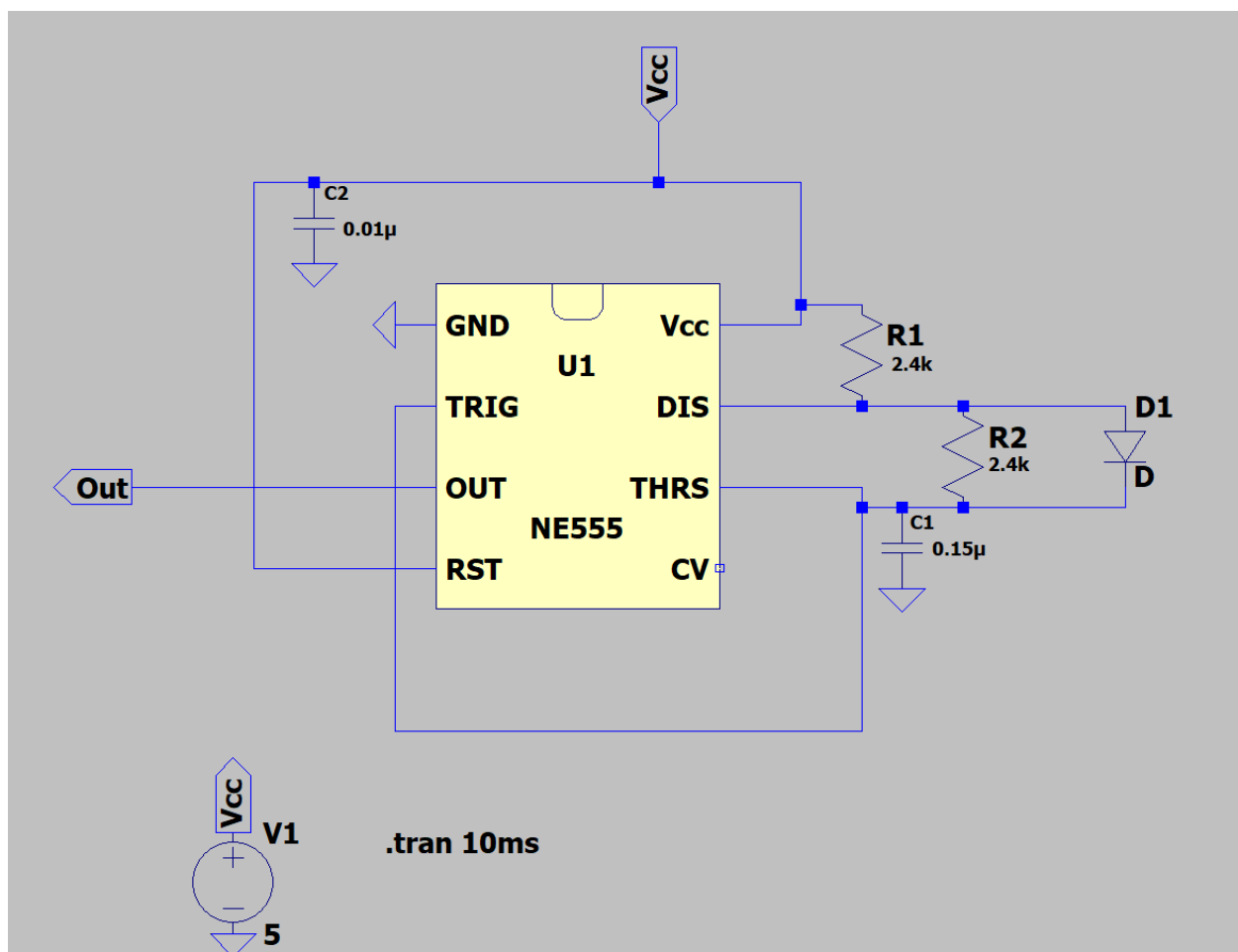


Figure 1 Schematic for Part 2

Simulation

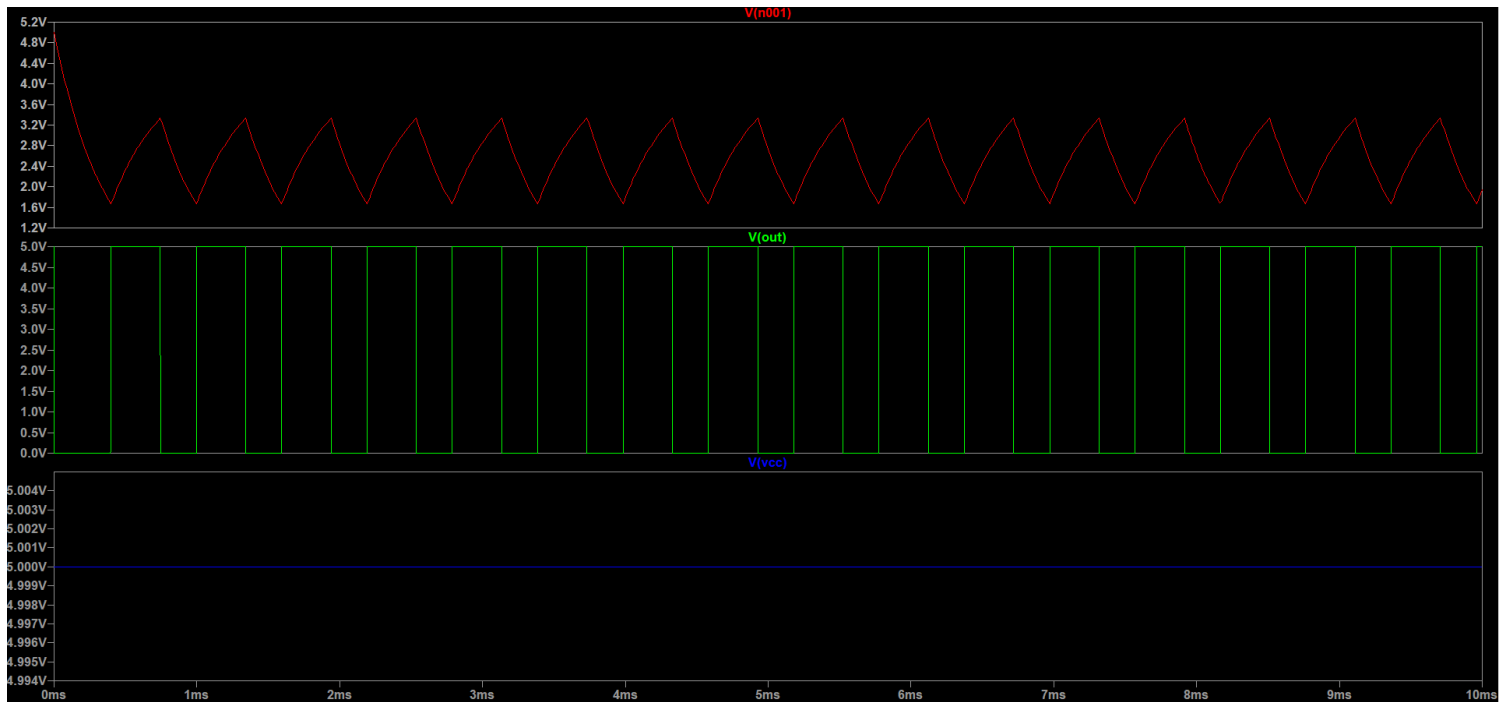


Figure 2 Simulation for Part 2

Frequency = 2kHz

Duty Cycle = 50 %

Therefore, Voltage changes 0.5ms in one time period

Part 3 :

Enrollment – 19114001

Running Monostable Multi-Vibrator which is negative edge – triggered and has a pulse of 1ms.

The pulse width duration $T_w = 1.1 (R * C)$, where $C = 0.01 \mu F$

$R = 9.1 K\Omega$

Schematic

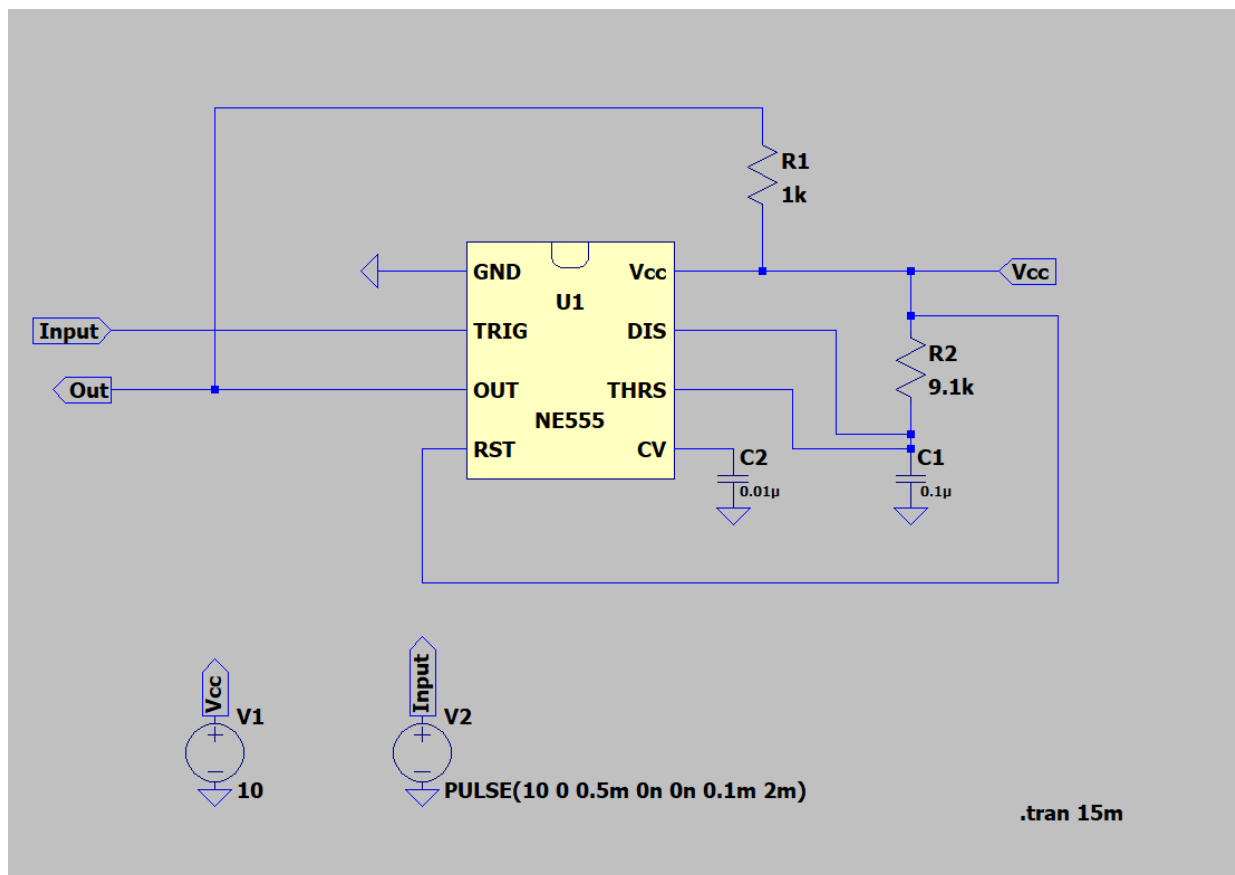


Figure 3 Schematic for Part 3

Simulation

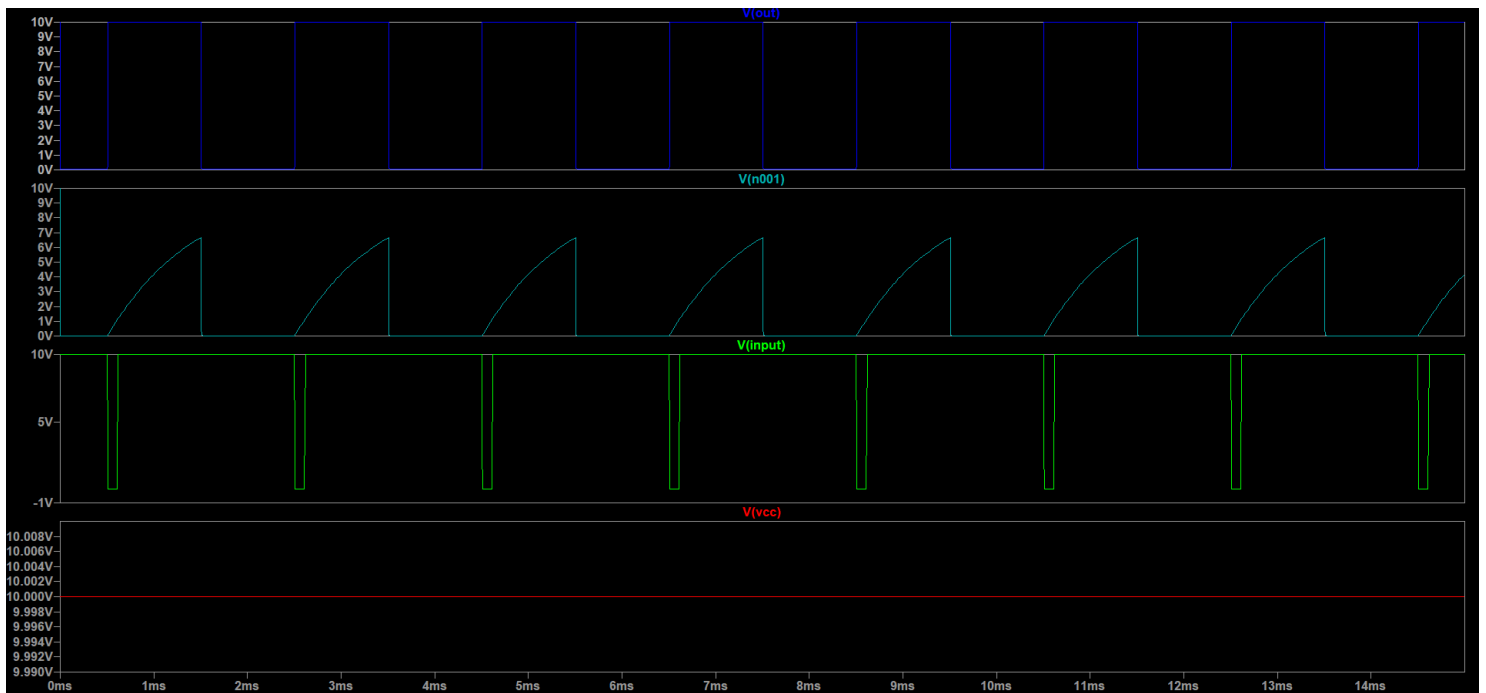


Figure 4 Simulation for Part 3